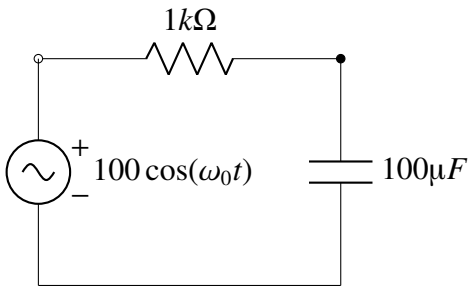


# GATE -BM 16

EE23BTECH11057 - Shakunaveti Sai Sri Ram Varun

**Question:** For the circuit given below, choose the angular frequency  $\omega_0$  at which voltage across capacitor has maximum amplitude?



**Solution:**